

Digital Systems Design and Laboratory

[Lab 1. Combinational Circuit Design]

Chung-Wei Lin

cwlin@csie.ntu.edu.tw

CSIE Department

National Taiwan University

Spring 2020

Outline

- ❑ **Introduction**
- ❑ Verilog Syntax
- ❑ Simulator Installation
- ❑ Demonstration
- ❑ Assignment


Hardware Description Language (HDL)

- ❑ Different from programming languages, they do not really "execute" at run time
- ❑ They describe hardware at different abstract levels
- ❑ Popular languages
 - Verilog, VHDL
- ❑ Logic synthesis
 - First convert HDL code into a netlist
 - Then place and route them to generate a set of masks (for IC) or a list of mapping and interconnections (for FPGA/CPLD)
- ❑ Simulation
 - Use a test bench to check if the behavior meets your requirements

Verilog: Switch Level Modeling

□ More details

 ➤ <https://www.slideshare.net/pradeepdevip/switch-level-modeling>




```
module inv(in, out);  
    output out;  
    input in;  
    supply0 a;  
    supply1 b;  
    nmos(out, a, in);  
    pmos(out, b, in);  
endmodule
```

Verilog: Gate Level Modeling

□ More details

 - [http://access.ee.ntu.edu.tw/course/logic_design_94first/941%20Verilog%20HDL\(Gate%20Level%20design\).pdf](http://access.ee.ntu.edu.tw/course/logic_design_94first/941%20Verilog%20HDL(Gate%20Level%20design).pdf)



```
module mux(out, sel, in1, in2);
    output out;
    input sel, in1, in2;
    wire iv_sel, a1_o, a2_o;
    not n1(iv_sel, sel);
    and a1(a1_o, in1, sel);
    and a2(a2_o, in2, iv_sel);
    or o1(out, a1_o, a2_o);
endmodule
```


Verilog: Behavioral Level Modeling

❑ Register-Transfer Level (RTL)

```
module mux(out, sel, in1, in2);  
    output out;  
    input sel, in1, in2;  
    reg out;  
    always @(sel, in1, in2)  
        if(sel==1)  
            out = in1;  
        else  
            out = in2;  
endmodule
```

```
module mux(out, sel, in1, in2);  
    output out;  
    input sel, in1, in2;  
    assign out = sel&in1  
        | ~sel&in2;  
endmodule
```
 
```
module mux(out, sel, in1, in2);  
    output out;  
    input sel, in1, in2;  
    assign out = sel?in1:in2;  
endmodule
```



Outline

- ❑ Introduction
- ❑ **Verilog Syntax**
- ❑ Simulator Installation
- ❑ Demonstration
- ❑ Assignment

Module

- ❑ Basic functional unit, can be instantiated in other modules

- `module <name>(<signal0>, <signal1>, <signal2>);`
 `output <signal0>;`
 `input <signal1>, <signal2>;`
 `// implementation`
`endmodule`

- `module <name>(output <signal0>, input <signal1>);`
 `reg <signal0>;`
 `// implementation`
`endmodule`

Data Types

□ **reg**

- Driven in a process block, may become a net or a register after synthesis

□ **wire**

- Driven outside a process block, becomes a net after synthesis
- Type of **input** and **output** is **wire** unless specified

□ **integer**

- Default to be 32 bit signed, usually used in test bench

□ **time**

- Equivalent to **reg[63:0]**

□ More details

- https://en.wikibooks.org/wiki/Programmable_Logic/Verilog_Data_Types

Integer Literals

- ❑ Binary (2): **4'b1011**
- ❑ Octal (8): **4'o13**
- ❑ Hexadecimal (16): **4'hb**
- ❑ Decimal (10): **4'd11 == -4'd5**
- ❑ Concatenation: **{2'b10, 2'b11} == 4'b1011**
- ❑ More details

➤ http://web.engr.oregonstate.edu/~traylor/ece474/beamer_lectures/verilog_number_literals.pdf

Concurrent and Sequential Statements

□ Concurrent statement

- "Executed" at the same time

wire a, b, c; assign b = a; assign c = b;

- Connect **wire b** to **wire a** and then connect **wire c** to **wire b**
 - If **a** changes from 0 to 1, **b** and **c** will change at the same instant

□ Sequential statement

- "Executed" one by one like programming languages

- But actually converted into equivalent concurrent statements

reg a, b, c; b = a; c = b;

- **[reg a] → [reg b] → [reg c]**

- If output of register **a** changes, **b** changes before **c**

- Sequential statements are only allowed in a process block

Assignments

❑ Continuous assignment

- Outside a process block

```
assign x = y & z; // continuous assignment  
// same as and a0(x, y, z), x cannot be a reg
```

❑ Blocking and non-blocking assignment

- Inside a process block

```
x = y; // blocking assignment  
a <= b; // non-blocking assignment  
b <= a; // a and b exchanges their values
```

Arrays

❑ Unpacked array (array)

```
reg an_unpacked_array[2:0];
```

❑ Packed array (vector)

```
reg[5:0] a_packed_array;
```

```
reg[0:5] a_packed_array; // same
```

```
reg[3:5] a_packed_array; // it's legal syntax!
```

❑ Icarus Verilog only supports 1-dimensional arrays

```
reg[5:0][4:0] two_dimensional_array[3:0][2:0]
```

```
// syntax error in Icarus Verilog
```

❑ More details

- <https://verificationacademy.com/forums/ovm/difference-between-packed-and-unpacked-arrays>

Indexing Arrays

□ Example

```
bit[3:0][4:0] how_to_index[1:0][2:0];
```

2

0

1

➤ `how_to_index[0][1][2] = 5'b00010;`

0

1

2

0	000000000000000000000000	0000000000 <u>00010</u> 00000	000000000000000000000000
	01234012340123401234	01234012340123401234	01234012340123401234
1	000000000000000000000000	000000000000000000000000	000000000000000000000000
	01234012340123401234	01234012340123401234	01234012340123401234

Operators

Verilog Operator	Name	Functional Group
[]	bit-select or part-select	
()	parenthesis	
!	logical negation	logical bit-wise reduction reduction reduction reduction reduction reduction
~	negation	
&	reduction AND	
	reduction OR	
~&	reduction NAND	
~	reduction NOR	
^	reduction XOR	
~^ or ^~	reduction XNOR	
+	unary (sign) plus	arithmetic arithmetic
-	unary (sign) minus	
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic arithmetic arithmetic
/	divide	
%	modulus	

+	binary plus	arithmetic arithmetic
-	binary minus	
<<	shift left	shift shift
>>	shift right	
>	greater than	relational relational relational relational
>=	greater than or equal to	
<	less than	
<=	less than or equal to	
==	logical equality	equality equality
!=	logical inequality	
===	case equality	equality equality
!==	case inequality	
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise bit-wise
^~ or ~^	bit-wise XNOR	
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional	conditional

❑ Note: no **a++** and **a+=1**

➤ Use **a=a+1** instead

➤ More details: <https://class.ece.uw.edu/cadta/verilog/operators.html>

Process Block (1/3)

□ **always** and **initial**

- Statements in **always** will be executed from time 0 and repeated forever
- **initial** is the same as **always** except that it only executes once

□ Example

- **always begin**
 <statements>
 end
- **always**
 <single statement>

Process Block (2/3)

□ Sensitivity list

- If **always** is followed by a **@**, the process will be executed once whenever the expressions in the list changes, instead of repeating from time 0

□ Example

- **always @(a or b) //old syntax**
- **always @(a, b)**
- **always @(a, posegde clk, negedge enable)**
- **always @a**
- **always @***

Process Block (3/3)

- ❑ Flow control

- ❑ Example

- `if(condition) begin`

- `<statements>`

- `end`

- `else begin`

- `<statements>`

- `end`

- `for() begin`

- `<statements>`

- `end`

- `while, case` are also supported

Delay

❑ Outside a process block

- **assign #10 a = b + c;**
 - The adder has 10 time units of propagation delay

❑ Inside a process block

- **#10;**
 - Delay 10 units
- **#10 a = b + c;**
 - Delay 10 units of time and evaluate **b+c**, assign it to **a**
- **a = #10 b + c;**
 - Evaluate **b+c** and execute the next statement, assign 10 time units later

❑ More details

- http://content.inflibnet.ac.in/data-server/eacharya-documents/53e0c6cbe413016f23443704_INFIEP_33/7/LM/33-7-LM-V1-S1__delay_modeling.pdf

Test Bench

❑ Macros and system tasks

- ``include <module>`
- ``define <parameter> <value>`
- ``timescale <unit>/<precision>`
- `$dumpfile("some_file.vcd");`
- `$dumpvars(<level>, <module>);`
 - Level = 0: variables in all levels
 - Level = 1: variables in only
 - Level = 2: variables in and one level below it
- `$display()`, `$write()`, `$monitor()`

References

- ❑ Summary of Synthesisable Verilog 2001 (2 pages)

- <https://www.cl.cam.ac.uk/teaching/0910/ECAD+Arch/files/verilogcheatsheet.pdf>

- ❑ Quick Reference for Verilog HDL (25 pages)

- <http://ece.eng.umanitoba.ca/undergraduate/ECE3610/Verilog%20Notes/VerilogQuickRef.pdf>

- ❑ Language reference

- <http://verilog.renerta.com/>

Outline

- ❑ Introduction
- ❑ Verilog Syntax
- ❑ **Simulator Installation**
- ❑ Demonstration
- ❑ Assignment

Icarus Verilog and GTKWave

❑ What is Icarus Verilog?

- <http://iverilog.icarus.com/>

❑ For Windows users

- <https://bleyer.org/icarus/>
- http://bleyer.org/icarus/iverilog-0.9.7_setup.exe (recommended)
 - Reminder: Run the installer as administrator!


❑ For Linux-like OS users

- `sudo apt-get update`
- `sudo apt-get install iverilog`
- `sudo apt-get install gtkwave`

❑ For Mac users

- Use `brew install` instead

After Downloading Successfully

 命令提示字元

```
Microsoft Windows [版本 10.0.18363.720]  
(c) 2019 Microsoft Corporation. 著作權所有，並保留一切權利。  
  
C:\Users\haha7>iverilog  
iverilog: no source files.  
  
Usage: iverilog [-EiSuvV] [-B base] [-c cmdfile|-f cmdfile]  
               [-g1995|-g2001|-g2005|-g2005-sv|-g2009|-g2012] [-g<feature>]  
               [-D macro[=defn]] [-I includedir]  
               [-M [mode=]depfile] [-m module]  
               [-N file] [-o filename] [-p flag=value]  
               [-s topmodule] [-t target] [-T min|typ|max]  
               [-W class] [-y dir] [-Y suf] [-l file] source_file(s)  
  
See the man page for details.
```


Commands and File Extensions

❑ Compile

- `> iverilog [-o compiled_file.vpp] source_file.v`
 - If no `-o` option provided, `a.out` will be generated

❑ Simulate

- `> vvp compiled_file.vvp`
 - A dump file will be generated if `$dumpfile("dump_file.vcd")` is called
 - vcd stands for Value Change Dump

❑ View waveform

- Open a new cmd window
- `> gtkwave`
- Open `dump_file.vcd` in GUI
- You can also use `gtkwave dump_file.vcd` in the same line

After Opening dump_file.vcd

The screenshot shows the GTKWave interface with the file `lab1.vcd` open. The interface is divided into several panels:

- SST (Source Tree):** Located on the left, it shows the project hierarchy. The `lab1_main` component is expanded, showing its internal components: `adder` and `adder_gl`. A yellow arrow points to this panel.
- Signals:** Located in the middle-left, it lists the signals in the project. The signals are: `a[2:0] = 000`, `b[2:0] = 000`, `c0 = 0`, and `s[2:0] = 000`. A yellow arrow points to this panel.
- Waves:** Located on the right, it displays the waveforms for the signals. The waveforms are shown for the time range from 0 to 217 seconds. The signals `a[2:0]`, `b[2:0]`, and `s[2:0]` are shown as 3-bit binary values. A yellow arrow points to this panel.
- Component List:** Located at the bottom left, it lists the components in the project. The components are: `reg a[2:0]`, `reg b[2:0]`, `reg c0`, `wire c3`, `wire c3_gl`, `integer delay`, `integer i`, `integer j`, `integer max_delay`, and `wire s[2:0]`. A yellow arrow points to this panel.

The waveforms show the following values:

Signal	0 sec	100 sec	200 sec	217 sec
<code>a[2:0]</code>	000	101	000	000
<code>b[2:0]</code>	000	011	000	000
<code>s[2:0]</code>	000	001	000	000

Hello World

□ Save as wow.v

➤ > iverilog -o wow.vvp wow.v && vvp wow.vvp

```
module wow();  
    wire out;  
    reg in;  
    not #3 n0(out, in);  
    integer i;  
    initial begin  
        $display("time / in out");  
        $monitor("%4d /  %b  %b", $time, in, out);  
        for(i=0; i<5; i=i+1) begin  
            $display("-----");  
            in <= i; // high bits will be truncated  
            #10;  
        end  
    end  
endmodule
```

Trouble Shooting

❑ For Windows users

- If you cannot run iverilog on command line, uninstall and run the installer as administrator
- If an error message pop up saying that some dll is missing, or the compiler executed but didn't generate any output file, try the latest version:
 - http://bleyer.org/icarus/iverilog-v11-20190327-x64_setup.exe

Outline

- ❑ Introduction
- ❑ Verilog Syntax
- ❑ Simulator Installation
- ❑ **Demonstration**
- ❑ Assignment

Half Adder and Full Adder

□ HA



➤ assign {C, S} = A + B;

□ FA

➤ assign {Cout, S} = A + B + Cin;

□ More details

  
➤ https://www.electronics-tutorials.ws/combination/comb_7.html



Ripple-Carry Adder (1/4)

□ Notice that carry_n depends on carry_{n-1}

➤ Where is the longest propagation path?

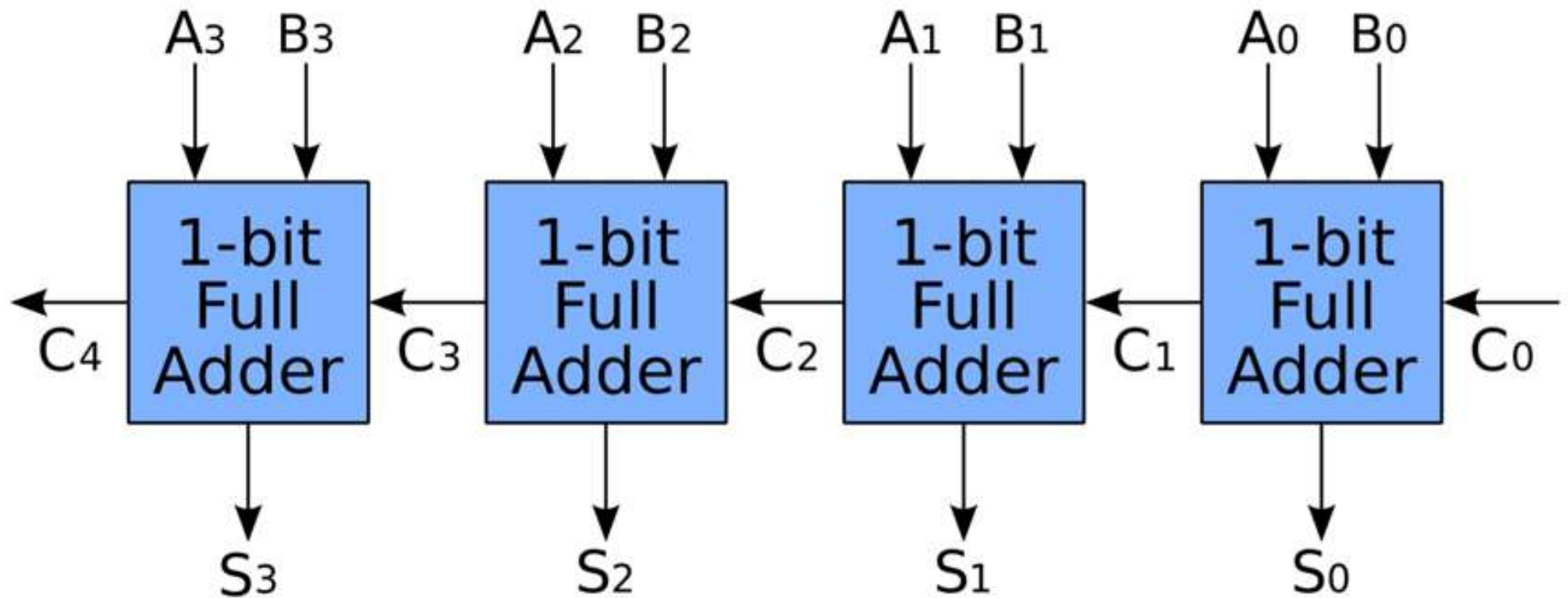

Ripple-Carry Adder (2/4)

□ Maximum delay

- Notice that $000+000+0 \rightarrow 111+000+1$ should cause the same delays



```
Command Prompt
C:\Users\mvnl424\Desktop\DSDL_lab\lab>iverilog -o lab1.vvp lab1.v && vvp lab1.vvp
VCD info: dumpfile lab1.vcd opened for output.
Maximum delay is 23 ticks on transition 000+000+0 --> 000+111+1
```


Ripple-Carry Adder (3/4)

Transition

```
Command Prompt
C:\Users\mvnl424\Desktop\DSDL_lab\lab>iverilog -o lab1.vvp lab1.v && vvp lab1.vvp
VCD info: dumpfile lab1.vcd opened for output.
time      a      b    c0 {c3 s}    gl
=====
  0 / 000 / 000 / 0 / 0000 / xxxx
 10 / 000 / 000 / 0 / 0000 / xxx0
 11 / 000 / 000 / 0 / 0000 / 0x00
 16 / 000 / 000 / 0 / 0000 / 0000
100 / 000 / 111 / 1 / 1000 / 0000
105 / 000 / 111 / 1 / 1000 / 0001
110 / 000 / 111 / 1 / 1000 / 0110
116 / 000 / 111 / 1 / 1000 / 0100
122 / 000 / 111 / 1 / 1000 / 0000
123 / 000 / 111 / 1 / 1000 / 1000
```

static hazards

Ripple-Carry Adder (4/4)


□ More details

➤ [https://en.wikipedia.org/wiki/Adder_\(electronics\)](https://en.wikipedia.org/wiki/Adder_(electronics))

Outline

- ❑ Introduction
- ❑ Verilog Syntax
- ❑ Simulator Installation
- ❑ Demonstration
- ❑ **Assignment**

Carry-Lookahead Adder (1/2)

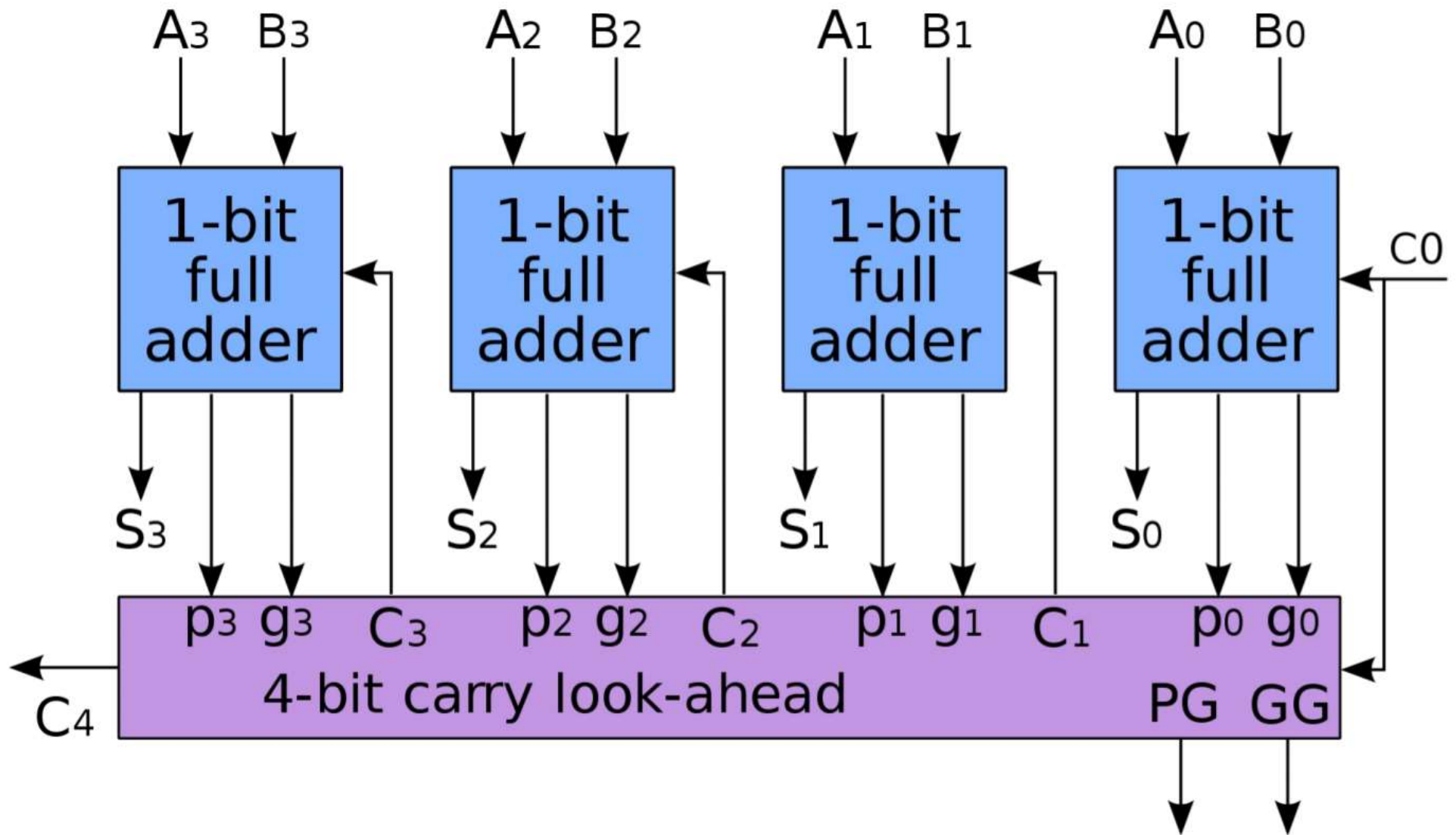

Carry-Lookahead Adder (2/2)

□ Carry lookahead method

➤ $G_i = A_i \cdot B_i$

➤ P_i can be either:

$$P_i = A_i \oplus B_i$$

$$P_i = A_i + B_i$$

□ Implementation details

➤ $C_1 = G_0 + P_0 \cdot C_0$

➤ $C_2 = G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1$

➤ $C_3 = G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + C_0 \cdot P_0 \cdot P_1 \cdot P_2$

➤ $C_4 = G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3 + C_0 \cdot P_0 \cdot P_1 \cdot P_2 \cdot P_3$

□ Reference

➤ https://en.wikipedia.org/wiki/Carry-lookahead_adder

Requirements (1/2)

- ❑ Implement a 3-bit adder **adder_rtl**
 - Use RTL modeling
- ❑ Implement a 3-bit carry-lookahead adder **cla_g1**
 - Use gate-level modeling
 - Only the gates provided in **gates.v** (with delays) are allowed to use

Requirements (2/2)

- ❑ Attach your source codes to your Homework 3
- ❑ Show the waveform of **cla_g1.S[2:0]** on input transitions
 - From $000 + 000 + 0$ to $001 + 000 + 1$
 - From $111 + 000 + 0$ to $000 + 111 + 0$
- ❑ Find the maximum propagation delay of **cla_g1**
 - And find one of the corresponding input transitions
- ❑ Assume that only 2-input gates are used, derive the number of levels needed in an n-bit carry-lookahead adder as a function of n
- ❑ Hand in along with Homework 3

Hints

- ❑ **adder_rt1** should be simple to implement
 - It can be implemented in one line
- ❑ The outputs of **adder_rt1** and **cla_g1** should be the same at steady state
 - If they are different, maybe there are some mistakes in **cla_g1** since it is more complicated
- ❑ Implement your adders in **adders.v**
 - The output and input signals are given
- ❑ Do not modify **gates.v**
- ❑ Only minor changes should be done to **lab1.v**
- ❑ Use system tasks and GTKWave to debug

Q&A